

GATE-2023, EC-35

EE23BTECH11033- JASWANTH KILLANA

Question:

In the circuit shown below, switch S was closed for a long time. If the switch is opened at $t=0$, the maximum magnitude of the voltage V_R in volts is. (round off to nearest integer).

solution :

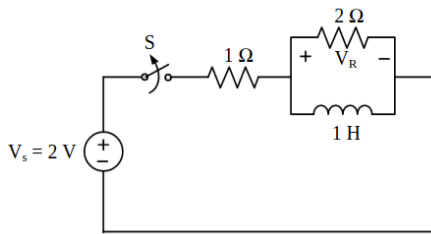


Fig. 0.

At, $t = 0^-$

inductor acts as wire
apply KVL in big loop

$$-2 + 1i(0^-) = 0$$

$$i(0^-) = 2A$$

here after $t=0$,

parameter	description	value
$i(0^-)$	current at $t < 0$	2
V_R	voltage across 2Ω	$-2i(t)$
L	inductance	1
$i(t)$	current in small loop after $t = 0$	$\frac{V_R}{2}$
$I(s)$	$i(t)$ in laplace	—

TABLE 0

INPUT PARAMETERS

KVL,

$$2i(t) + L \frac{di}{dt} = 0 \quad (4)$$

apply laplace transform,

$$2I(s) - Li(0^-) + LsI(s) = 0 \quad (5)$$

$$\Rightarrow I(s) = \frac{i(0^-)}{s+2} \quad (6)$$

$$I(s) = \frac{2}{s+2} \quad (7)$$

applying inverse laplace transform

$$I(t) = 2 \cdot e^{-2t} \quad (8)$$

$$V_R = -2I(t) \quad (9)$$

$$\Rightarrow V_R = -4 \cdot e^{-2t} \quad (10)$$

As,

$$t \rightarrow 0 \quad (11)$$

$$e^{-2t} \rightarrow 1 \quad (12)$$

$$|V_R(\max)| = 4 \quad (13)$$

This is the simulation for V_R vs time

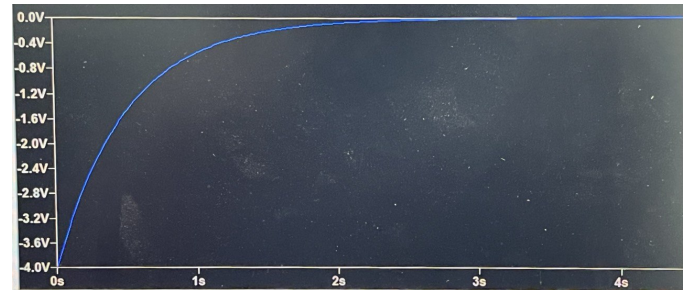


Fig. 0.

The magnitude of graph is max at $t = 0$ of magnitude 4V and then decreases with t . Which supports the solution by doing laplace transform method.