

GATE-2023, EC-35

EE23BTECH11033- JASWANTH KILLANA

Question:

In the circuit shown below, switch S was closed for a long time. If the switch is opened at $t=0$, the maximum magnitude of the voltage V_R in volts is. (round off to nearest integer).

solution : here at $t < 0$, switch is closed

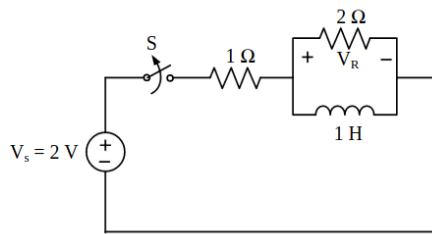


Fig. 0.

parameter	description	value
$i(0^-)$	current at $t < 0$	—
$i(0^+)$	current at $t > 0$	—
V_R	voltage across 2Ω	—
L	inductance	1
$i(t)$	current in small loop after $t = 0$	$\frac{V_R}{2}$

TABLE 0

INPUT PARAMETERS

after $t = 0$, switch is opened
for an inductor

$$i(0^+) = i(0^-) \quad (1)$$

apply KVL before $t < 0$
inductor acts as wire

-

$$-2V + i(0^-) = 0 \quad (2)$$

$$\Rightarrow i(0^-) = i(0^+) = 2A \quad (3)$$

after $t = 0$;

KVL in loop of inductor and 2Ω resistor

let i be current in the loop in anti clockwise

direction

$$L \frac{di}{dt} = -2i \quad (4)$$

$$\Rightarrow \frac{di}{i} = \frac{-2dt}{L} \quad (5)$$

$$\int_{i(0^+)}^{i(t)} \frac{1}{i} di = \int_0^t \frac{-2}{L} dt \quad (6)$$

$$\ln\left(\frac{i(t)}{2}\right) = -2t \quad (7)$$

$$\Rightarrow i(t) = 2 \cdot e^{-2t} \quad (8)$$

$$V_R = 2i(t) V \quad (9)$$

$$= 4 \cdot e^{-2t} V \quad (10)$$

$$\text{As, } t \rightarrow \infty \quad (11)$$

$$e^{-2t} \rightarrow 1 \quad (12)$$

$$|V_R(\max)| = 4V \quad (13)$$